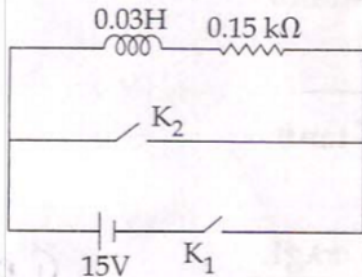



10. An inductor ($L=0.03\text{H}$) and a resistor ($R=0.15\text{ k}\Omega$) are connected in series to a battery of 15V EMF in a circuit shown below. The key K_1 has been kept closed for a long time. Then at $t=0$, K_1 is opened and key K_2 is closed simultaneously. At $t=1\text{ms}$, the current in the circuit will be : ($e^5 \approx 150$)



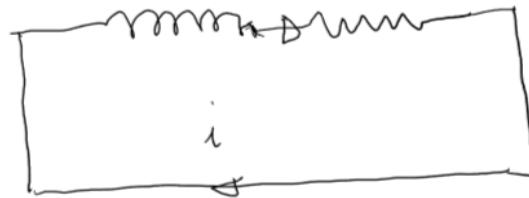- (1) 6.7 mA
- (2) 0.67 mA
- (3) 100 mA
- (4) 67 mA ← correct

After $t=0$, circuit is an LI circuit

$L = 0.03\text{H}$ $R = 0.15\text{ k}\Omega$



$$L \frac{di}{dt} + Ri = 0$$

$$\int_{i_0}^i \frac{di}{i} = \int_{t=0}^t -\frac{R}{L} dt$$

At $t=0$, $i = i_0$

$$\Rightarrow \ln \frac{i}{i_0} = -\frac{R}{L} t \Rightarrow \boxed{i = i_0 e^{-(R/L)t}}$$

Given $t = 1\text{ms}$, $i = ?$

$$\Rightarrow i = 0.1 \times e^{-\left(\frac{150}{0.03}\right) \times 10^{-3}}$$

$$i_0 = \frac{15\text{V}}{0.15\text{ k}\Omega} = 0.1\text{A}$$

$$i = 0.1 e^{-5} \approx \frac{0.1}{150} \approx 0.67\text{ mA}$$