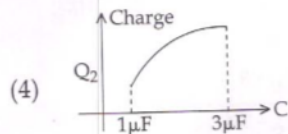
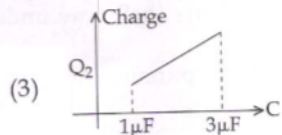
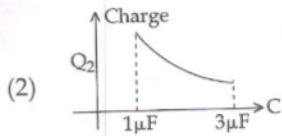
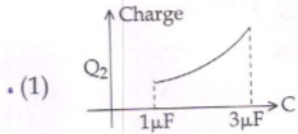
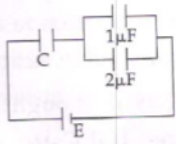


12. In the given circuit, charge Q_2 on the $2\mu\text{F}$ capacitor changes as C is varied from $1\mu\text{F}$ to $3\mu\text{F}$. Q_2 as a function of ' C ' is given properly by: (figures are drawn schematically and are not to scale)



Correct

Writing the eqn for the circuit which includes $2\mu\text{F}$ capacitor

$$E - \frac{q}{C} - \frac{Q_2}{2} = 0$$

(q is charge on ' C ' capacitor)

$$\therefore Q_2 = 2E - \frac{2q}{C}$$

\therefore as C increases, Q_2 increases

as $C \rightarrow \infty$, $Q_2 \rightarrow 2E$

Therefore as C increases, curve for Q_2 asymptotically approaches $2E$.

Therefore (4) is correct